

**Government College of Engineering, Amravati**  
(An Autonomous Institute of Government of Maharashtra)

**Sixth Semester B. Tech.**  
**(Computer Science and Engineering)**

**Summer – 2016**

**Course Code: Switching Theory and Logic Design**

**Course Name: CSU601**

**Time: 2 Hrs. 30 Min.**

**Max. Marks: 60**

**Instructions to Candidate**

- 1) All questions are compulsory.
- 2) Assume suitable data wherever necessary and clearly state the assumptions made.
- 3) Diagrams/sketches should be given wherever necessary.
- 4) Use of logarithmic table, drawing instruments and non-programmable calculators is permitted.
- 5) Figures to the right indicate full marks.

**1. Solve any two:**

- (a) Show type classification available in VHDL and explain scalar data type in brief. 6m
- (b) Explain case, wait and loop sequential statements in detail with example. 6m
- (c) Design VHDL code for 9 bit parity generator circuit 6m

**2. Solve:**

- (a) Write short note on: 4m
  - i) Explicit visibility with clauses
  - ii) Operator overloading

- (b) Write VHDL code for: 8m  
i) 1bit full adder using dataflow modeling  
ii) synchronous D-type flip-flop triggered on the rising edge of the clock signal using behavioural modelling

3. **Solve:**

- (a) Simplify the following Boolean function: 4m  
 $F(A,B,C,D) = \Sigma_m(1,2,4,7,8,11,13,14)$

- (b) Find all the prime implicants for the Boolean functions given and determine which are essential PI  $F(A,B,C,D) = \Sigma_m(0,1,3,4,5,7,13,15)$ , using Tabulation method 6m

- (c) Prove that the compliment of a function is equal to complementing a function using dual method. 2m

4. **Solve any one:**

- (a) Design BCD to 7 segment LED code convertor. 12m

- (b) (i) Design BCD to Excess-3 code convertor 6m

- (ii) Design VHDL code for 3:8 decoder using Data flow modeling and logic circuit along with its truth table 6m

5. **Solve**

- (a) Design 3 bit synchronous up counter using J-K flip flop. 6m

- (b) What are shift register? Explain bi-directional shift register with parallel load in detail 6m