

**Government College of Engineering, Amravati**  
**Department of Electronics**

Course Code: ETU302  
Course Name: CDIT

CT-I

Time: 1 hr  
Marks: 15

Attempt any **THREE**

- Q.1 Suggest the DC bridge used for the measurement of low resistance without causing the effect of contact resistance and prove that how the effect of contact resistance eliminated? 05
- Q.2 Define transducer with classification. Enlist and Explain the different parameter required for selection of electrical transducer. 05
- Q.3 How stray capacitances affecting bridge measurement and how to eliminate its effect? 05
- Q.4 Explain Hay's Bridge. Find the value of series inductance ( $L_x$ ) and resistance ( $R_x$ ) in network for  $R_2=10k\Omega$ ,  $R_1=2k\Omega$ ,  $C_1=1\mu F$ ,  $R_3=1k\Omega$  and  $\omega =3000$  rad/sec. 05

$$R_x \cdot R_1 = R_2 \cdot R_3$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_x}$$

$$R_x = \frac{R_2 R_3}{R_1}$$

$$L_x = \frac{C_1 R_2 R_3}{1 + \omega^2 R_1^2 R_3^2}$$

$$R_x = \frac{\omega^2 R_1^2 R_3^2}{1 + \omega^2 R_1^2 R_3^2}$$