

Government college of Engineering
(An Autonomous Institute of Maharashtra)

Marks:-15
sub:-EDC (ETU303)

CT:-I
Set(A)

Date :- 06/08/15
Time:-1Hr.


Q1) Solve the following questions.

(A) With the help of circuit diagram explain the working of a half wave rectifier. Show the relevant waveforms. Obtain expression for efficiency of rectification. 5M

(B) A FWR employs two vacuum diodes, the internal resistance of each diode may be assumed constant at 500Ω . The transformer r.m.s. secondary voltage from centre tap to each of secondary end is 300V and load has a resistance of 2000Ω . Find (i) d.c. power o/p (ii) a.c. power i/p (iii) rectification efficiency 5M OR

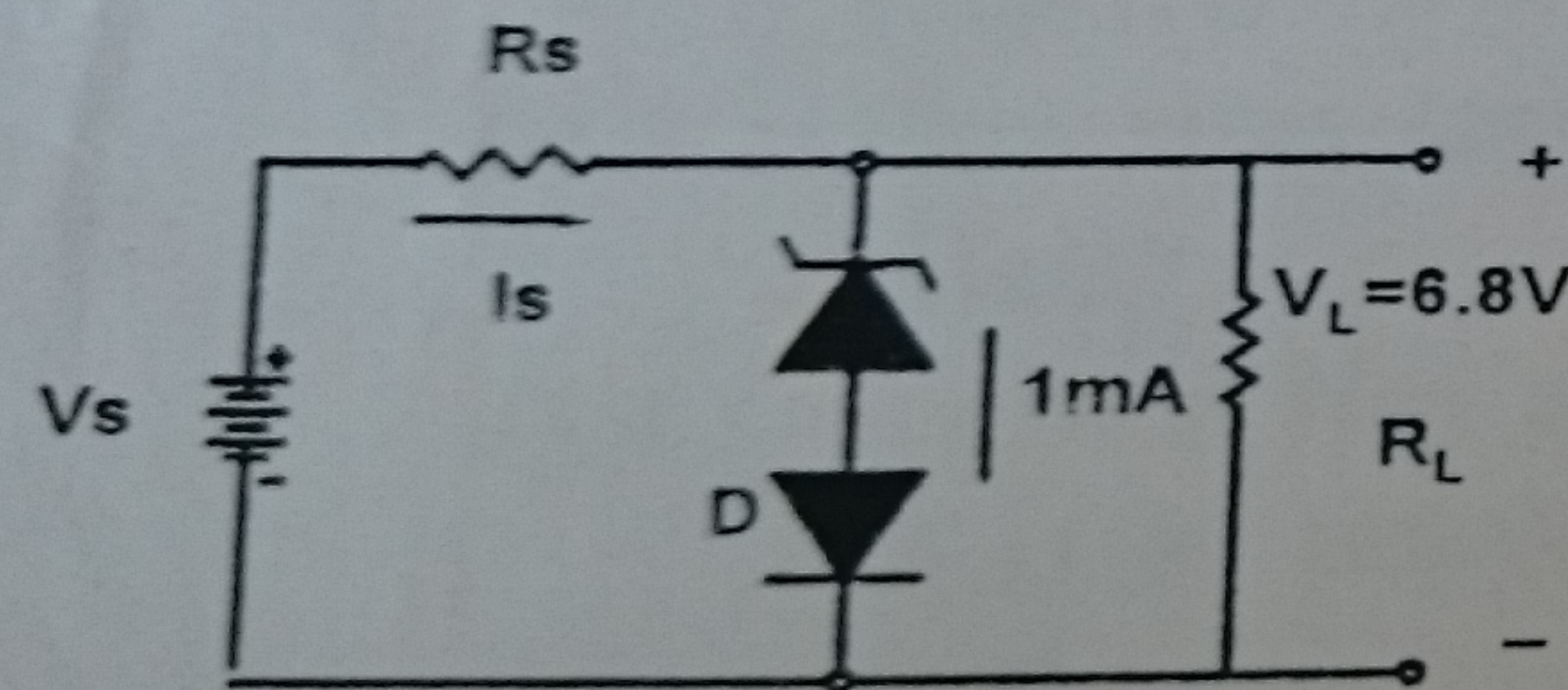(C) Design a zener voltage regulator shown in figure to meet following specifications:

Load voltage 6.8V, source voltage V_s is $\pm 20\%$ and the load current is $30\text{ mA} \pm 50\%$. The zener requires a minimum current of 1mA to breakdown. The diode D has a forward conducting voltage of 0.6V. 5M



(D) What is the necessity of having filter in power supplies? Explain with diagrams how R-C filter improves the output of rectifiers. 5M OR

(E) Explain working principle of (i) Schottky diode (ii) Tunnel diode. Give their characteristics and typical applications. 5M

$$V = \frac{I}{R} \quad V = IR$$