

Government College of Engineering, Amravati
Department of Electronics Engineering
Class Test- I

Course Code: ETU304

Course Name: Digital Electronics

Date: 07/08/2015

Duration: 01 Hr

Max. Marks: 15

Time: 03:00 - 04:00

All questions are compulsory; marks of three best answers out of four will be considered

- 1] Using K-map write down the following expressions for the given function; 05
 $Y(\alpha, \beta, \gamma, \delta) = \sum m\{1, 3, 5, 7, 8, 10, 12, 14\} + d(0, 15)$ and comment implementing which expression is better? Why? a. Standard SoP, b. Reduced SoP c. Standard PoS, d. Reduced PoS
- 2] Design a $\langle 8 \ 4 \ 2 \ 1 \rangle$ code to $\langle 8 \ 4 \ 2 \ -1 \rangle$ code convertor; which code is more useful? Why? 05
- 3] Describe the process of error detection and correction using Hamming codes for 7 message bits and required parity bits using even parity. 05
- 4] Describe Universal Gates; design Ex-OR Gate using NAND and NOR gates. 05