

Government college of Engineering, Amravati

("An Autonomous institute of government of Maharashtra")

Date: 21/09/2015

Course Code- ETU301 (NA)

Time: 1 hour

Marks: 15M

All Figures are at back side of paper.

- Q.1** Solve any 2
- a. Derive the equivalent Y parameter for the 2 parallel connected network and find Z parameter for the given fig.1 5M
- b. Find the Y and H parameter for given network in fig.2 5M
- c. i) Calculate Y parameter for given fig.3 3M
- ii) What is characteristic impedance Calculate. Z_0 for given T-Network in fig.4 2M
- Q.2** i) Calculate T Parameter for fig.5 3M
- ii) Design a constant K low pass filter (π and T section) having cut-off frequency of 2 KHz to operate with terminal load resistance of 500 ohm. 2M